

EE 210L — Digital Circuits and Logic Design Lab

Lab 1: Logic Gates and Truth Tables

Name: _____ Date: _____

Partner(s): _____ Section: _____

Fill in every measured value. Record the voltage you actually measured, not the value you expected. Show your work where a calculation is asked for. Submit this report on Canvas — see Canvas for the deadline and grading rubric.

Part 1 — Power Supply Setup

Measured power supply voltage: _____ V

Current limit setting: _____ mA

Part 2 — Gate Truth Tables

For each gate, set the inputs with jumper wires, measure the output with the DMM, and convert the measurement to a logic level ($HIGH \geq 2.0\text{ V}$, $LOW \leq 0.8\text{ V}$).

2.1 AND — 74LS08

A	B	Measured V_{out} (V)	Logic Output	Expected Output
0	0			
0	1			
1	0			
1	1			

2.2 OR — 74LS32

A	B	Measured V_{out} (V)	Logic Output	Expected Output
0	0			
0	1			
1	0			
1	1			

2.3 NOT — 74LS04

A	Measured V_{out} (V)	Logic Output	Expected Output
0			
1			

2.4 NAND — 74LS00

A	B	Measured V_{out} (V)	Logic Output	Expected Output
0	0			
0	1			
1	0			
1	1			

2.5 NOR — 74LS02

Remember that the 74LS02 output is pin 1 and its inputs are pins 2 and 3.

A	B	Measured V_{out} (V)	Logic Output	Expected Output
0	0			
0	1			
1	0			
1	1			

2.6 XOR — 74LS86

A	B	Measured V_{out} (V)	Logic Output	Expected Output
0	0			
0	1			
1	0			
1	1			

Did every gate match the truth table you predicted in your pre-lab? If any did not, explain what was wrong and how you fixed it.

Part 3 — Floating Input

With one input of the 74LS08 tied HIGH and the other left disconnected:

Voltage measured at the floating input pin: _____ V

Voltage measured at the output: _____ V

Which band of §3.1 does the floating input fall into (valid HIGH, valid LOW, or undefined)? Why should you never leave an input floating in a real design?

Part 4 — Inverter Chain and Level Restoration

Input at pin 1	V at pin 1 (V)	V at pin 2 (V)	V at pin 4 (V)
Logic 0			
Logic 1			

Explain what the second inverter does to the signal level coming out of the first one.

Part 5 — NAND as a Universal Gate

5.1 NOT from NAND

Draw or paste your circuit diagram in the box. Label every pin number you used.

Figure 1: NOT gate built from a single NAND gate.

A	Measured V_{out} (V)	Logic Output
0		
1		

5.2 AND from NAND

 


Figure 2: AND gate built from NAND gates only.

A	B	Measured V_{out} (V)	Logic Output
0	0		
0	1		
1	0		
1	1		

5.3 OR from NAND



Figure 3: OR gate built from NAND gates only.

A	B	Measured V_{out} (V)	Logic Output
0	0		
0	1		
1	0		
1	1		

How many NAND gates did each circuit take? Why does being able to build NOT, AND, and OR out of one gate type matter to someone manufacturing a chip?

This image shows a blank sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.