

EE 210L: Digital Circuits and Logic Design Lab

Lab 6: Latches and Flip-Flops

Name: _____ Date: _____

Partner(s): _____ Section: _____

The 74LS73 uses V_{CC} on pin 4 and GND on pin 11. Confirm your wiring before applying power. Submit this report on Canvas, where you will also find the deadline and grading rubric.

Part 1: NAND SR Latch

$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$	Behavior (set / reset / hold / forbidden)
1	1			
0	1			
1	1			
1	0			
1	1			
0	0			

1.1 Forbidden State: Release Test

Take both inputs LOW, then release both at once. Record where the latch lands. Repeat five times.

Trial	1	2	3	4	5
Q after release					

Was the result the same every time? Explain what determines the outcome.

Part 2: 74LS279 Quad SR Latch

$\bar{S}$	$\bar{R}$	Measured V at Q (V)	Q	Behavior
1	1			
0	1			
1	0			
0	0			

Part 3: D Flip-Flop (74LS74)

3.1 Clocked Operation

D	Q after several clock edges	$\bar{Q}$
1		
0		

3.2 Transparency Check

Clock held at	Does Q follow changes on D?
HIGH (static)	
LOW (static)	

What does this prove about the difference between a latch and an edge-triggered flip-flop?

3.3 Asynchronous Clear

With the clock running and D held HIGH, pulsing CLR LOW caused Q to:

Did it wait for a clock edge? _____

Part 4: Propagation Delay

Paste your oscilloscope capture showing the clock edge and the Q transition with cursors placed.

 


Figure 1: Clock-to-Q propagation delay measurement.

Measured t_{PLH} or t_{PHL} (clock edge to 50% of Q): _____ ns

Datasheet value for the 74LS74: _____ ns

If they differ, suggest a reason.

Part 5: JK Flip-Flop (74LS73)

J	K	Observed Q behavior	Expected behavior	Match?
0	0			
0	1			
1	0			
1	1			

Part 6: Toggle Mode and Frequency Division

Paste your capture showing the clock and Q together.

 


Figure 2: Clock and Q of a toggle flip-flop.

Signal	Measured frequency	Ratio to clock
Clock		1
Q of first flip-flop		
Q of second flip-flop		

A chain of toggle flip-flops is counting something. What?

Discussion and Conclusions

Address at least: why the SR forbidden state is genuinely unpredictable rather than merely undefined on paper, why synchronous systems are built from edge-triggered flip-flops rather than latches, and what setup and hold time violations would do to your circuit.

This image shows a blank sheet of white paper with horizontal ruling lines. The lines are evenly spaced and extend across the width of the page. There are no margins, text, or other markings on the paper.