

EE 210L: Digital Circuits and Logic Design Lab

Lab 7: Shift Registers and Counters

Name: _____ Date: _____

Partner(s): _____ Section: _____

The 74LS73 uses V_{CC} on pin 4 / GND on pin 11, and the 74LS90 uses V_{CC} on pin 5 / GND on pin 10. Confirm both before applying power. Submit this report on Canvas, where you will also find the deadline and grading rubric.

Part 1: Ripple Counter

Signal	Measured frequency	Ratio to clock
Clock		1
1Q (stage 1)		
2Q (stage 2)		

Paste the capture showing that 2Q changes after 1Q rather than with it.

 


Figure 1: Ripple delay between counter stages.

Measured delay from the 1Q edge to the 2Q edge: _____ ns

Estimated worst-case delay for an 8-bit ripple counter built the same way: _____ ns

Part 2: Synchronous Counter (74LS163)

Count	QD	QC	QB	QA	Decimal	RCO
1						
2						
3						
4						
5						
6						
7						
8						
9						
10						
11						
12						
13						
14						
15						
16						

RCO asserts at state _____. Output frequencies at 10 kHz clock: QA = _____,
QD = _____

Part 3: Mod-10 Counter

Outputs Nanded to detect state 9: _____ and _____

Count	QD	QC	QB	QA	Decimal
1					
2					
3					
4					
5					
6					
7					
8					
9					
10					

Why does state 10 never appear, even briefly? What would be different on a counter with an asynchronous clear?

Part 4: Decade Counter (74LS90)

Count	QD	QC	QB	QA	Decimal
1					
2					
3					
4					
5					
6					
7					
8					
9					
10					

Effect of taking R0(1) and R0(2) HIGH together:

Part 5: Universal Shift Register (74LS194)

5.1 Parallel Load and Hold

Mode (S1 S0)	After clock edge	QA	QB	QC	QD
1 1 (load 1011)	1st				
0 0 (hold)	after several				

5.2 Shift Right (S1 S0 = 01, SR SER = 0)

Clock edge	QA	QB	QC	QD
start				
1				
2				
3				
4				

5.3 Shift Left (S1 S0 = 10, SL SER = 0)

Clock edge	QA	QB	QC	QD
start				
1				
2				
3				
4				

Part 6: Ring Counter

Clock edge	QA	QB	QC	QD
start (loaded 1000)				
1				
2				
3				
4				
5				
6				
7				
8				

Part 7: Johnson Counter

Clock edge	QA	QB	QC	QD
start (cleared)				
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				

7.1 States per Flip-Flop

Counter type	States from 4 flip-flops	Decoding logic needed per state
Ring		
Johnson		
Binary		

Discussion and Conclusions

Address at least: what decoding glitches are and why a ripple counter produces them, why a synchronous clear matters for the mod-10 design, and the trade-off between ring, Johnson, and binary counters.

This image shows a blank sheet of white paper with horizontal ruling lines. The lines are evenly spaced and extend across the width of the page. There are no margins, text, or other markings on the paper.